

Counter 4-bit

Name: dhruv subandh

Roll No.:7

Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity Counter_4 is
    port(
        rst : in  STD_LOGIC;
        pr : in  STD_LOGIC;
        clk : in  STD_LOGIC;
        clk_div : inout STD_LOGIC;
        dir : in  STD_LOGIC;
        Q : out  STD_LOGIC_VECTOR (3 downto 0)
    );
end Counter_4;

architecture Behavioral of Counter_4 is
    signal Qtemp : STD_LOGIC_VECTOR (3 downto 0) := "0000";
    signal Counter : STD_LOGIC_VECTOR (26 downto 0) := (others => '0');
begin
    process(rst,pr,clk_div,dir)
    begin
        if rst='1' then
            Qtemp <= (OTHERS => '0');
        elsif pr='1' then
            Qtemp <= (OTHERS => '1');
        elsif falling_edge(clk_div) then
            if dir = '1' then
```

```

        if Qtemp < 15 then
            Qtemp <= Qtemp + 1;
        else
            Qtemp <= "0000";
        end if;
    else
        if Qtemp > 0 then
            Qtemp <= Qtemp - 1;
        else
            Qtemp <= "1111";
        end if;
    end if;
end if;
end process;
Q <= Qtemp;

process(clk)
begin
    if clk'event and clk = '1' then
        counter <= counter + 1;
    end if;
end process;

clk_div <= counter(0);
end Behavioral;

```

TestBench:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

```

entity Counter_4_TB is

end Counter_4_TB;

architecture Behavioral of Counter_4_TB is

component Counter_4 is

port(

rst : in STD_LOGIC;

pr : in STD_LOGIC;

clk : in STD_LOGIC;

clk_div : inout std_logic;

dir : in STD_LOGIC;

Q : out STD_LOGIC_VECTOR (3 downto 0)

);

end component;

signal rst : std_logic := '0';

signal pr : std_logic := '0';

signal clk : std_logic := '0';

signal clk_div : std_logic := '0';

signal dir : std_logic := '0';

signal Q : std_logic_vector(3 downto 0);

begin

uut: Counter_4 port map(rst, pr, clk, clk_div, dir, Q);

clk_process : process

begin

clk <= '0';

wait for 10 ns;

clk <= '1';

```

        wait for 10 ns;
    end process;

    stim_proc : process
    begin
        rst <= '1';
        wait for 20 ns;
        rst <= '0';

        --Up Counter
        dir <= '1';
        wait for 500 ns;

        pr <= '1';
        wait for 20 ns;
        pr <= '0';

        --Down Counter
        dir <= '0';
        wait for 300 ns;

        wait;
    end process;
end Behavioral;

```

Constraints:

```

set_property PACKAGE_PIN L1 [get_ports {Q[3]}]
set_property PACKAGE_PIN P1 [get_ports {Q[2]}]
set_property PACKAGE_PIN N3 [get_ports {Q[1]}]
set_property PACKAGE_PIN P3 [get_ports {Q[0]}]

```

```


set_property IOSTANDARD LVCMOS33 [get_ports {Q[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Q[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Q[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Q[0]}]
set_property PACKAGE_PIN W5 [get_ports clk]
set_property PACKAGE_PIN U16 [get_ports clk_div]
set_property PACKAGE_PIN R2 [get_ports dir]
set_property PACKAGE_PIN T1 [get_ports pr]
set_property PACKAGE_PIN U1 [get_ports rst]
set_property IOSTANDARD LVCMOS33 [get_ports clk]
set_property IOSTANDARD LVCMOS33 [get_ports clk_div]
set_property IOSTANDARD LVCMOS33 [get_ports dir]
set_property IOSTANDARD LVCMOS33 [get_ports pr]
set_property IOSTANDARD LVCMOS33 [get_ports rst]

```

```

set_property CLOCK_DEDICATED_ROUTE FALSE [get_nets pr_IBUF]

```

 

MOD 25 Counter

Name: dhruv subandh

Roll No.:7

Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity mod25 is
    Port (
        rst : in STD_LOGIC;
        pr  : in STD_LOGIC;
        clk : in STD_LOGIC;
        clk_div : inout STD_LOGIC;
        dir : in STD_LOGIC;
        Q   : out STD_LOGIC_VECTOR(4 downto 0)
    );
end mod25;
architecture mod25_arch of mod25 is
    signal Qtemp : STD_LOGIC_VECTOR(4 downto 0) := "00000";
    signal Counter : STD_LOGIC_VECTOR (27 downto 0) := (others => '0');
begin
    process(rst, pr, clk, dir)
    begin
        if rst = '1' then
            Qtemp <= (others => '0');

        elsif pr = '1' then
            Qtemp <= (others => '1');

        elsif falling_edge(clk) then
```

```

    if dir = '1' then --UP counting
        if Qtemp < 24 then
            Qtemp <= Qtemp + 1;
        else
            Qtemp <= "00000";
        end if;
    else --DOWN counting
        if Qtemp > 7 then
            Qtemp <= Qtemp -1;
        else
            Qtemp <= "11111";
        end if;
    end if;
end if;

end process;

Q <= Qtemp;

process(clk)
begin
    if clk'event and clk = '1' then
        counter <= counter + 1;
    end if;
end process;

clk_div <= counter(0);
end mod25_arch;

```

Test Bench:

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

```



```

entity mod25_tb is
end mod25_tb;

architecture Behavioral of mod25_tb is

    --Component Declaration for the Unit Under Test (UUT)
    component mod25
        Port (
            rst : in STD_LOGIC;
            pr  : in STD_LOGIC;
            clk : in STD_LOGIC;
            clk_div : inout STD_LOGIC;
            dir : in STD_LOGIC;
            Q   : out STD_LOGIC_VECTOR(4 downto 0)
        );
    end component;

    --Signals to connect to the UUT
    signal rst : STD_LOGIC := '0';
    signal pr  : STD_LOGIC := '0';
    signal clk : STD_LOGIC := '0';
    signal clk_div : STD_LOGIC := '0';
    signal dir : STD_LOGIC := '1'; --default: up count
    signal Q   : STD_LOGIC_VECTOR(4 downto 0);

begin

    --Instantiate the Unit Under Test (UUT)
    uut: mod25
        port map (
            rst => rst,
            pr  => pr,
            clk => clk,
            clk_div => clk_div,
            dir => dir,

```

```

        Q => Q
    );
--Clock generation: 10 ns period (falling edge sensitive)
clk_process : process
begin
    while true loop
        clk <= '1';
        wait for 5 ns;
        clk <= '0';
        wait for 5 ns;
    end loop;
end process;
--Stimulus process
stim_proc: process
begin
    --Initial reset
    rst <= '1';
    wait for 20 ns;
    rst <= '0';
    wait for 20 ns;
    --Up count for a few cycles
    dir <= '1'; --count up
    wait for 300 ns;
    --Now preset
    pr <= '1';
    wait for 20 ns;
    pr <= '0';
    wait for 20 ns;
    --Down count
    dir <= '0';

```

```

wait for 300 ns;

--Apply reset again

rst <= '1';

wait for 20 ns;

rst <= '0';

--End simulation

wait;

end process;

end Behavioral;

```



Universal Shift Register

Name: dhruv subandh

Roll No.:7

Code:

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity USR_Code is
port (
    clk : in std_logic;
    clk_div : inout std_logic;
    rst : in std_logic;
    load : in std_logic;
    mode : in std_logic_vector (1 downto 0);
    si : in std_logic;
    pi : in std_logic_vector (3 downto 0);
    so : out std_logic;
    po : out std_logic (3 downto 0)
);
end USR_Code;

architecture beh of USR_Code is
    signal shift_reg : std_logic_vector(3 downto 0);
    signal counter : std_logic_vector (26 downto 0) := (others => '0');
begin
    process(clk)
    begin
        if clk'event and clk = '1' then
            if rst = '1' then
                counter <= (others => '0');
            else
```

```

        counter <= counter + 1;
    end if;
end if;

end process;

clk_div <= counter(0);

process(clk_div, rst, load)
begin
    if rst = '1' then
        shift_reg <= (others => '0');
    elsif
        clk_div'event and clk_div = '1' then
            case mode is
                when "00" =>
                    shift_reg(3 downto 1) <= shift_reg(2 downto 0);
                    shift_reg(0) <= si;
                    so <= shift_reg(3);
                when "01" =>
                    shift_reg(3 downto 1) <= shift_reg(2 downto 0);
                    shift_reg(0) <= si;
                    po <= shift_reg;
                when "10" =>
                    if load = '0' then
                        shift_reg <= pi;
                    else
                        shift_reg(3 downto 1) <= shift_reg(2 downto 0);
                    end if;
                    so <= shift_reg(3);
                when "11" =>
                    po <= pi;
                when others => null;
            end case;
        end if;
    end process;
end process;

```

```
end beh;
```

TestBench:

```
library ieee;
```

```
use ieee.std_logic_1164.all;
```

```
use ieee.std_logic_unsigned.all;
```

```
entity USR_TB is
```

```
end USR_TB;
```

```
architecture beh of USR_TB is
```

```
    component USR_Code is
```

```
    port (
```

```
        clk : in std_logic;
```

```
        clk_div : inout std_logic;
```

```
        rst : in std_logic;
```

```
        load : in std_logic;
```

```
        mode : in std_logic_vector (1 downto 0);
```

```
        si : in std_logic;
```

```
        pi : in std_logic_vector (3 downto 0);
```

```
        so : out std_logic;
```

```
        po : out std_logic_vector (3 downto 0));
```

```
    end component;
```

```
    signal clk, clk_div, rst, load, si, so : std_logic := '0';
```

```
    signal mode : std_logic_vector(1 downto 0);
```

```
    signal pi, po : std_logic_vector (3 downto 0);
```

```
begin
```

```
    uut: USR_Code PORT MAP (clk, clk_div, rst, load, mode, si, pi, so, po);
```

```
    clk_process : process
```

```
begin

    clk <= '0';

    wait for 10 ns;

    clk <= '1';

    wait for 10 ns;

end process;
```

```
stim_process : process

begin

    rst <= '1';

    wait for 20 ns;

    rst <= '0';
```

```
mode <= "00";

    si <= '1';

    wait for 200 ns;

    si <= '0';

    wait for 200 ns;
```

```
mode <= "01";

    si <= '1';

    wait for 100 ns;

    si <= '0';

    wait for 200 ns;
```

```
mode <= "10";

    load <= '0';

    pi <= "1110";

    wait for 100 ns;

    load <= '1';

    wait for 300 ns;
```

```
mode <= "11";

    pi <= "1010";
```



```
wait for 50 ns;
```

```
pi <= "1010";
```

```
wait for 50 ns;
```

```
wait;
```

```
end process;
```

```
end beh;
```

